

# Multicycle Nios II Processor

**Learning Goal:** Simple multicycle processor architecture.


**Requirements:** FPGA4U, Quartus II Web Edition and ModelSim-Altera.

## 1 Introduction


In this exercise you will implement a multicycle Nios II processor. You will use some of the components you built in the previous sessions. You will implement it step-by-step, beginning with a **CPU** that executes a few basic instructions, and extending it progressively to cover all the requested functionalities of the Nios II.
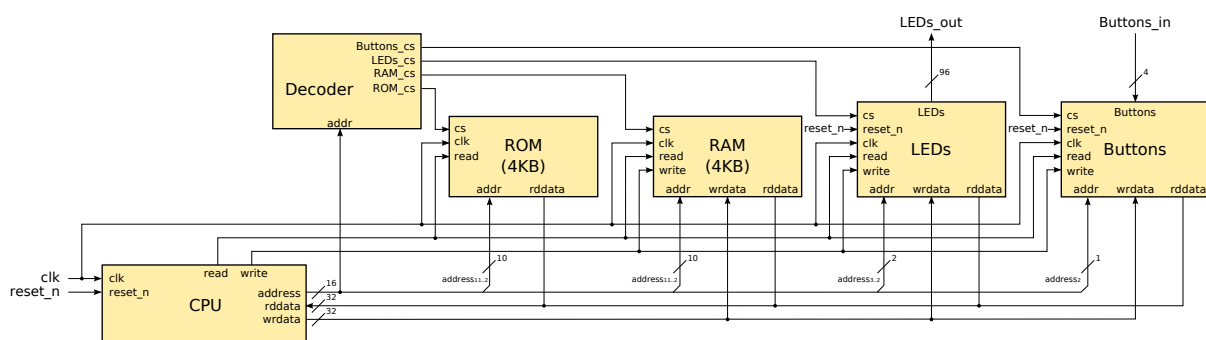
## 2 Multicycle CPU Description

The first implementation of the **CPU** will only execute several ALU operations (e.g., **addi**, **and**) and the **ldw** and **stw** instructions. A **break** instruction will also be used to stop the execution of the program. The **CPU** is connected into the same system you built for the **memories** project with an additional **Button** module, which interfaces the four buttons of the FPGA4U:



 To execute an instruction, the multicycle **CPU** will need 4 to 5 cycles, depending on the instruction. The following figure is the state machine of the controller of the **CPU**. It illustrates the different steps of the execution of an instruction:




During **FETCH1** and **FETCH2**, the **CPU** reads the next instruction to execute. During **DECODE**, the **CPU** identifies the instruction and determine the next state. During the next states the instruction is executed. We will call these last states *Execute* states.

The next subsections describe each state, and progressively introduce the internal units and signals of the **CPU**.
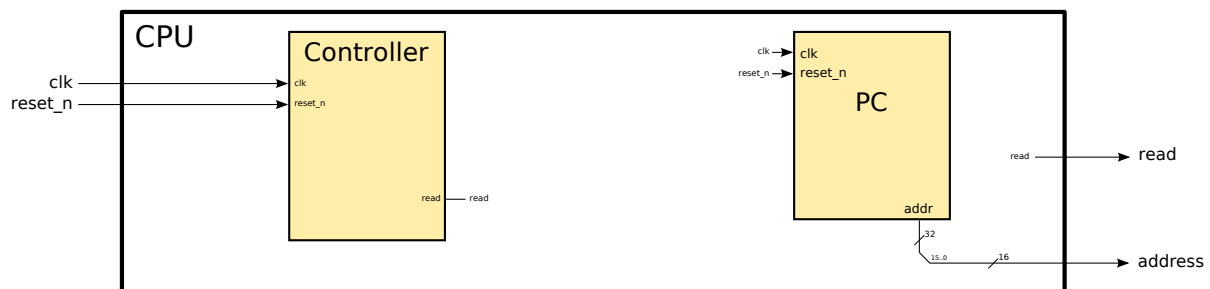
## 2.1 FETCH1

During this first state of the execution, the address of the next instruction and the signal **read** are set to start a new read process. The instruction word will be available during the next cycle.




The **Controller** controls the state machine. The input **reset.n** initializes the state machine to **FETCH1**. The **PC** holds the address of the next instruction. The address is stored in a 16-bit register. The address must always be valid, thus the two least significant bits should remains at '0'.

The first version of the **CPU** will be purely sequential: the next address is the current address incremented by 4.

- Input **clk** is the clock signal.
- Output **addr** is the current 16-bit register value extended to 32 bits. The 16 most significant bits are set to 0.
- Input **reset.n** initializes the address register to 0.
- Input **en** (see **FETCH2** figure) enables the **PC** to switch to the next address (i.e., **addr+4** for the moment).
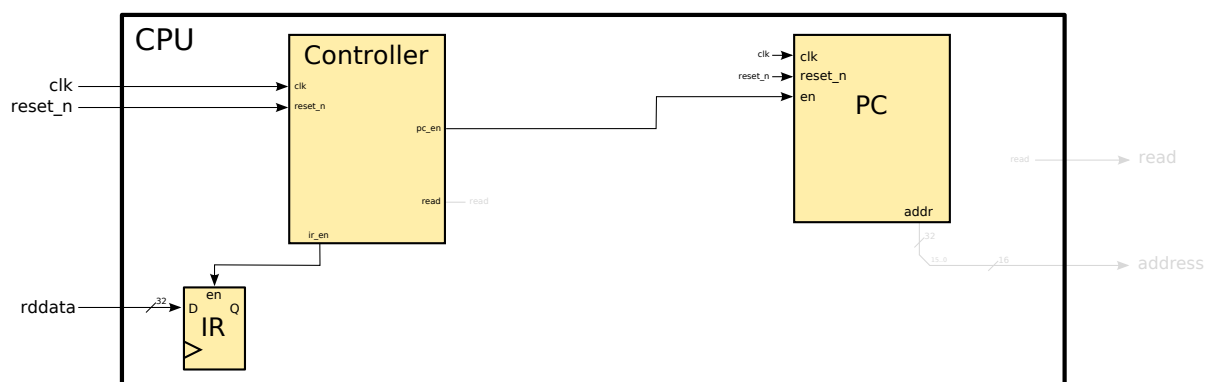
## 2.2 FETCH2

During this state, the instruction word is read from the input **rddata**, and saved in a register. The **Controller** enables the **PC**, so that it increments the address by 4.




The **Instruction Register (IR)** is a 32-bit register that stores the instructions coming from the memory.

- The input **clk** is the clock signal.
- The input **en** enables to write the input **D** in the register at the next rising edge of the clock.
- The output **Q** is the current value of the register.
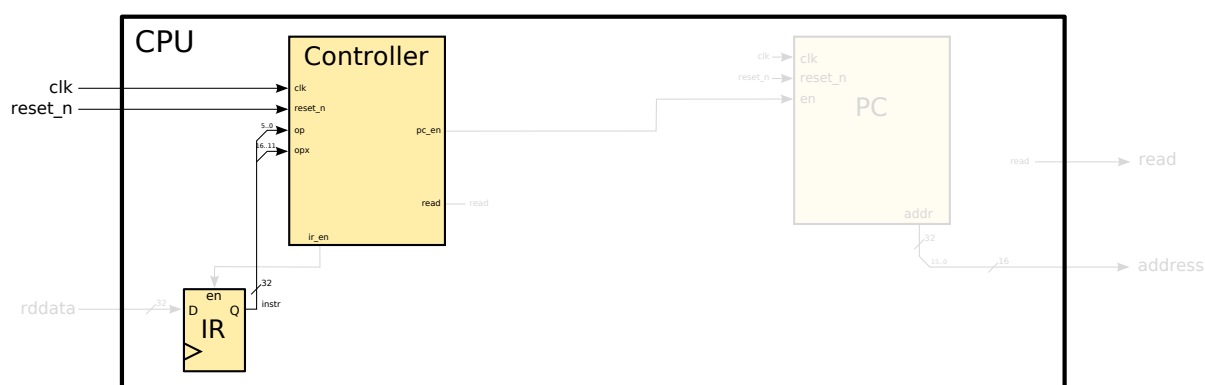
## 2.3 DECODE

During this state, the **Controller** reads the opcode of the instruction to identify the current instruction, and determines the next state. The Nios II instructions are progressively described in the following subsections.




## 2.4 I.OP

The **I.OP** state executes operations between a register and an *immediate* value that is embedded in the instruction word, and saves the result in a second register. Such instructions with a 16-bit *immediate* embedded value are **I-type** instructions (for Immediate type). The general **I-type** instruction format is detailed below.

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0								
A								B								IMM16																OP							

The fields **A** and **B** are register addresses. In most of the cases, **A** is a register operand, and **B** is the destination register. The field **IMM16** is the 16-bit *immediate* value. The field **OP** is the opcode of the instruction.

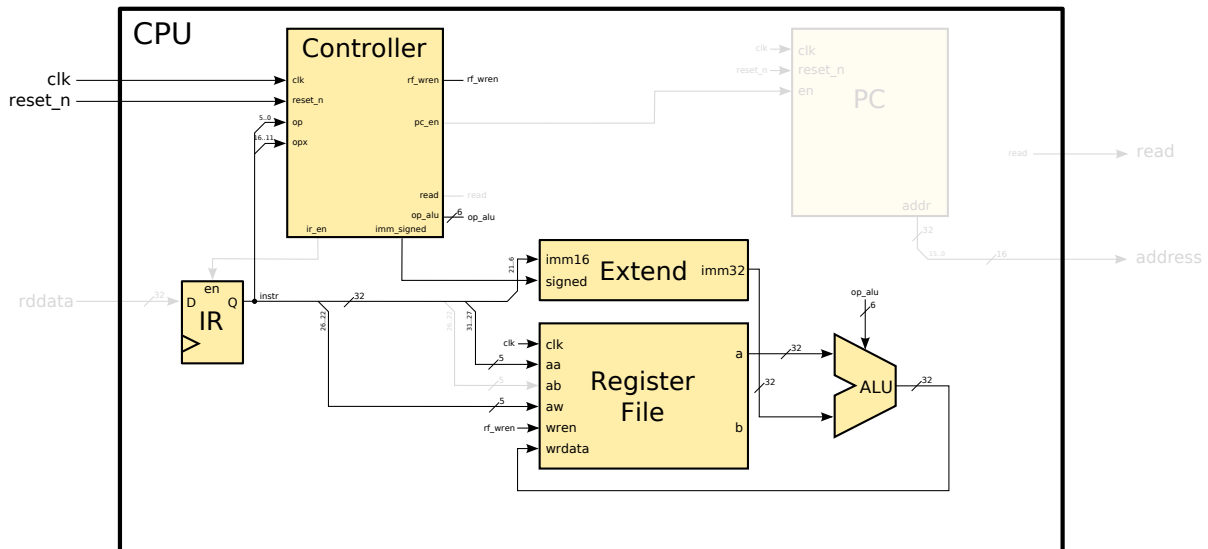During the state **I\_OP**, the **op\_alu** signal is set by the **Controller** to perform the required operation in the ALU. The result of the **ALU** is saved in the **Register File**.



The **Register File** and the **ALU** are the same units that you have implemented during the previous sessions. The **Extend** unit extends the width of the 16-bit field **IMM16** to 32 bits. The sign is extended or not depending on the signal **signed**.

The **Controller** selects the operation to execute in the **ALU** with the signal **op\_alu**. The **op\_alu** signal depends on the current instruction (e.g., an *addition* for **addi**, **stw** and **ldw**, a *logical AND* for **and**, or a *logical right shift* for **srl**).

The **ALU** opcode is summarized in the following table.

Operation	Operation Type	Opcode
$A + B$	Add/Sub	000 $\phi\phi\phi$
$A - B$		001 $\phi\phi\phi$
$A \geq B$ (signed)	Comparison	011001
$A < B$ (signed)		011010
$A \neq B$		011011
$A = B$		011100
$A \geq B$ (unsigned)		011101
$A < B$ (unsigned)		011110
$A \text{ nor } B$	Logical	10 $\phi\phi$ 00
$A \text{ and } B$		10 $\phi\phi$ 01
$A \text{ or } B$		10 $\phi\phi$ 10
$A \text{ xor } B$		10 $\phi\phi$ 11
$A \text{ rol } B$	Shift/Rotate (Optional)	11 $\phi$ 000
$A \text{ ror } B$		11 $\phi$ 001
$A \text{ sll } B$		11 $\phi$ 010
$A \text{ srl } B$		11 $\phi$ 011
$A \text{ sra } B$		11 $\phi$ 111

$\phi$  = don't care


## 2.5 R\_OP

The R\_OP state executes operations between two registers, and saves the result in a third register. Such instructions with three register addresses are **R-type** instructions (for Register type). The general **R-type** instruction format is detailed below.

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
A					B					C					OPX					IMM5					0x3A						

The fields **A**, **B** and **C** are register addresses. In most of the cases, **A** and **B** are register operands, and **C** is the destination register. The field **IMM5** is a small 5-bit *immediate* value that is only used by a few **R-type** instructions. The field **OP** is always set to 0x3A for **R-type** instructions, this is the way to identify them. The field **OPX** is an extension of the field **OP** and is the actual opcode of the **R-type** instructions.

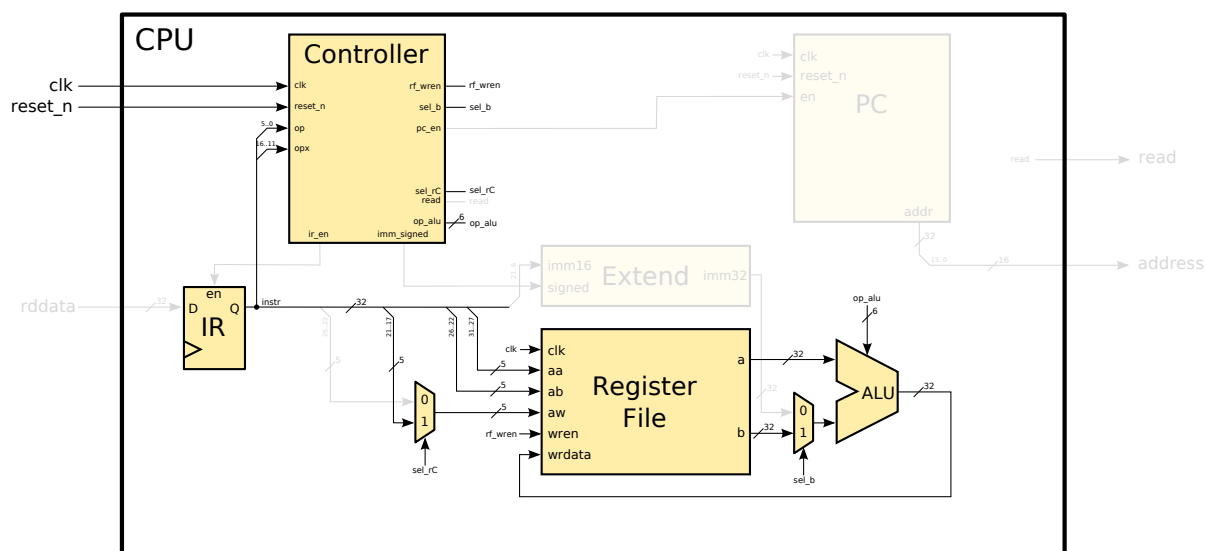During the state R\_OP, the signal **op\_alu** is set by the **Controller** to perform the required operation in the ALU. Register **b** is selected as the second operand, and the result of the ALU is saved in the **Register File**.




The multiplexer controlled by the signal **sel.b** selects the second operand of the ALU: either register **b** (for R-type instructions) or the immediate value (for I-type instructions). The multiplexer controlled by the **sel.rC** signal selects the write address (**aw**) from either the **B** (for I-type instructions) or **C** (for R-type instructions) instruction field.

## 2.6 LOAD

The **ldw** instruction is a **I-type** instruction with **OP**=0x17.


31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
A					B					IMM16												0x17									

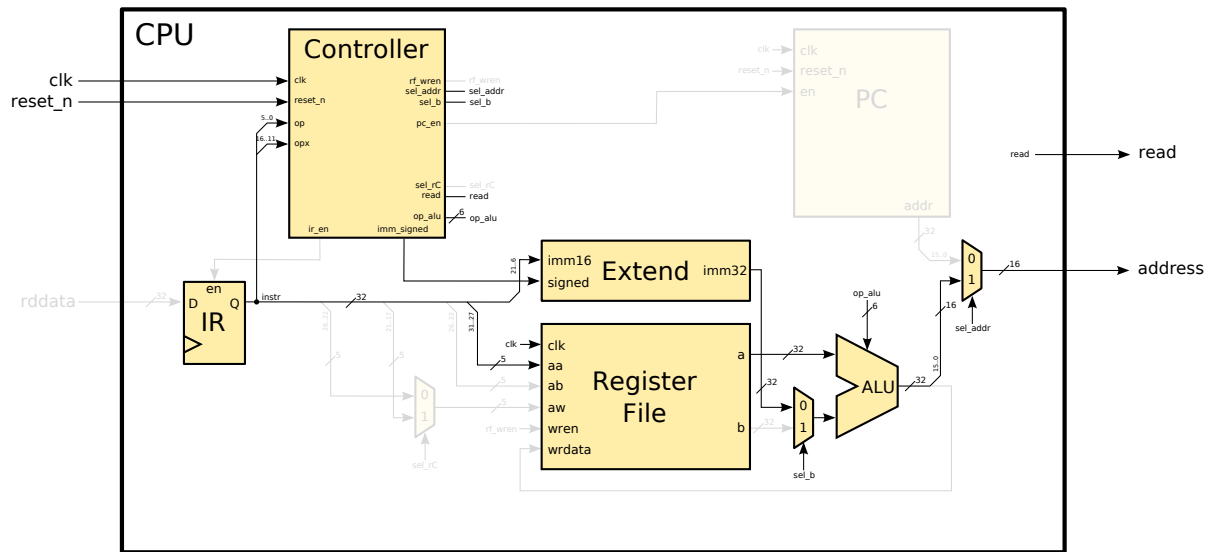The load operation takes 1 more cycle than the other instructions. This is caused by the read process, which has a 1-cycle latency. During the state **LOAD1**, the address to read is computed by the ALU (adding the signed *immediate* value to **a**) and the signal **read** is set to start a read process. The read value will be available during **LOAD2**.



The multiplexer controlled by the signal **sel\_addr** selects the memory address from either the **PC** address or the result of the **ALU**.

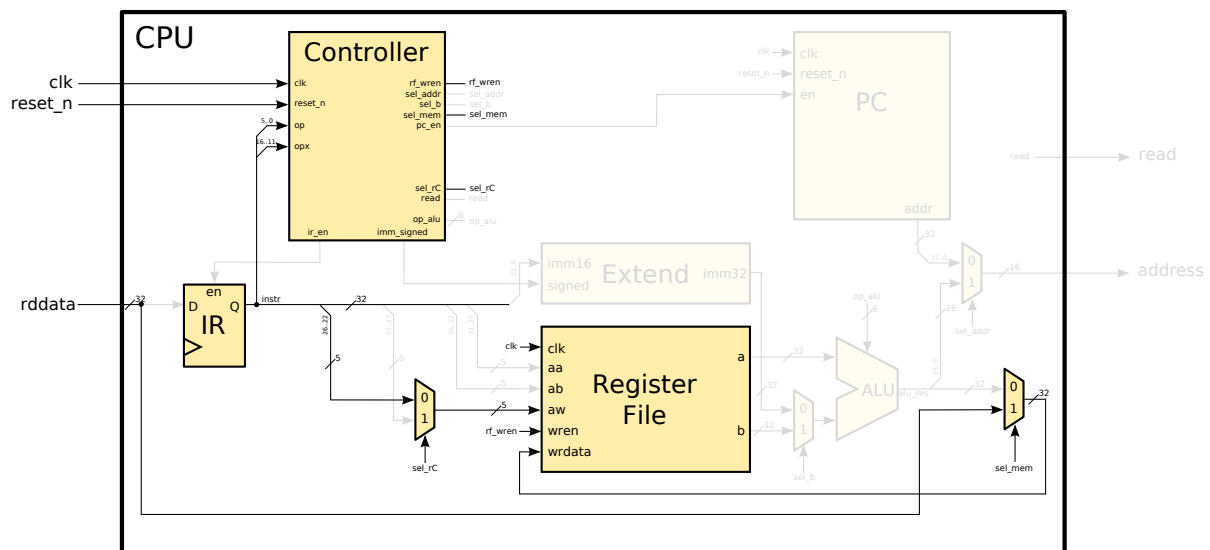During the state **LOAD2**, the memory data is written to the **Register File** at the address specified by **B**.




The multiplexer controlled by the signal **sel\_mem** selects the data to write to the **Register File** from either the result of the **ALU** or the **rddata** input.

## 2.7 STORE

The **stw** instruction is a **I-type** instruction with **OP**=0x15.

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
A					B					IMM16												0x15									

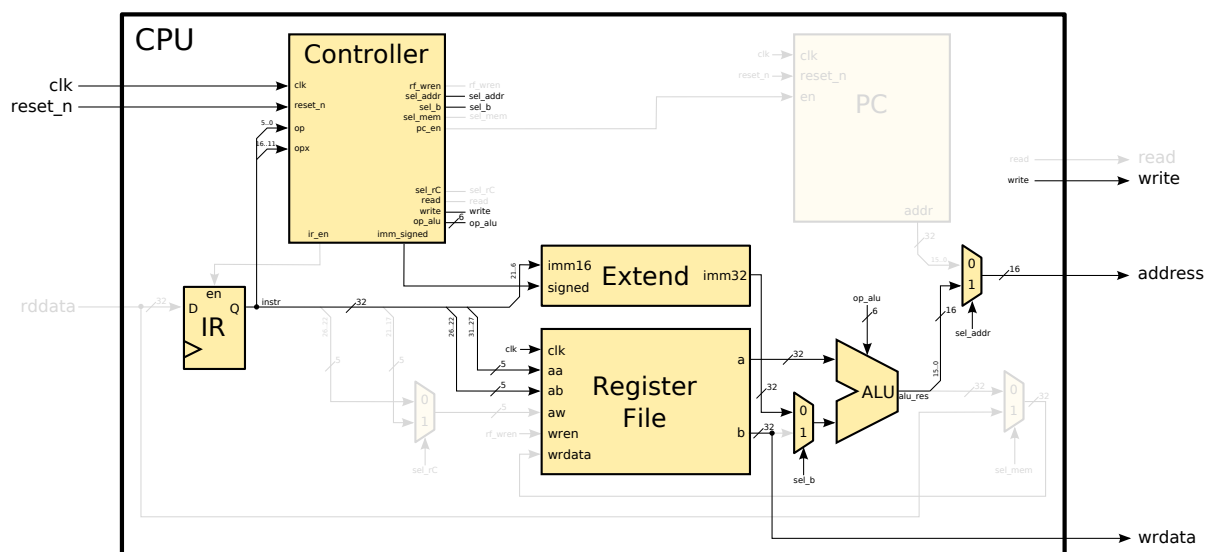During the state **STORE**, the **ALU** computes the memory address as for a **ldw** instruction, and the **Controller** activates the **write** output signal to start a write process. The data to write is held in the register **b**.



## 2.8 BREAK

The **break** instruction is a **R-type** instruction with **OPX=0x34**.

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x00	0x3A

This instruction will be used to stop the CPU execution (note that this is not the official purpose of this instruction). The state **BREAK** is simply a dead end.

## 3 Exercise

- Download the project template.
- Open the Quartus project, and open the `system.bdf` file. Notice that the CPU is connected into the same system that you used during the project **memories**.
- For this exercise, you will use some units you should have implemented during the previous sessions. Copy the following files into the **vhdl** folder of this project, and make sure the filenames and entities matches:
  - For the **ALU**, copy all the VHDL files in the **vhdl** folder of your **ALU** project.
  - For the **Register File**, copy the `register_file.vhd` of your project **register\_file**.
  - For the memory system, copy the `ROM.vhd`, `RAM.vhd`, `LEDs.vhd`, `ROM_Block.vhd` and `decoder.vhd` files from your **memories** project.
  - Modify the Decoder to add a new `cs_buttons` output that is activated when we access the **Buttons** module (addresses 0x2030 to 0x2034).

If you were not able to finish some of these design files during the previous exercise sessions, you can use their corresponding solution from the **solution** folder. However, you are strongly encouraged to take the time to finish them by yourself, or at least to fully understand them.

- The general architecture of the **CPU** is already given in the `CPU.bdf` file. This file contains the architecture for the complete version of the CPU. You will find extra control signals in addition to the ones discussed until now. Ignore them for the moment (set them to 0 while you implement the **Controller**).

- Implement the multiplexers: `mux2x5`, `mux2x16` and `mux2x32`. These multiplexers only differ on their bitwidth.
- Implement the **Extend** unit.
- Implement the **IR**.
- Implement a first version of the **PC**. In this first version, the next address is always the current address incremented by 4.
- Implement a first version of the **Controller**. In this first version, it should be able to decode the following instructions:

Instruction	State	Type	OP	OPX	Description
<b>and</b> <code>rC, rA, rB</code>	R_OP	R-type	0x3A	0x0E	$rC \leftarrow rA \text{ AND } rB$
<b>srl</b> <code>rC, rA, rB</code>	R_OP	R-type	0x3A	0x1B	$rC \leftarrow (\text{unsigned})rA \gg rB_{4..0}$
<b>addi</b> <code>rB, rA, imm</code>	I_OP	I-type	0x04	-	$rB \leftarrow rA + (\text{signed})imm$
<b>ldw</b> <code>rB, imm(rA)</code>	LOAD	I-type	0x17	-	$rB \leftarrow \text{Mem}[rA + (\text{signed})imm]$
<b>stw</b> <code>rB, imm(rA)</code>	STORE	I-type	0x15	-	$\text{Mem}[rA + (\text{signed})imm] \leftarrow rB$
<b>break</b>	BREAK	R-type	0x3A	0x34	Stops the program execution

Implement the described state machine, which controls all the control signals except **op\_alu**. The **op\_alu** signal is independent of the current state (i.e. it should be stateless) and should be generated in a separated process that is only dependent on **OP** and **OPX**. This will simplify the introduction of additional operations.

- Compile the Quartus project and correct the syntax errors.

To test the CPU, you will write a short machine language program.

- Download the Nios2Sim simulator from the web page of the course.
- The simulator is a Java executable (`.jar`). If you want to execute it on your own machine, make sure you have installed a Java Runtime Environment (JRE). For more details go to the Java web site: <http://www.java.com>.
- Double click on the `nios2sim.jar` file to run it.
- Copy the following Nios II assembly code to the Nios2Sim text editor, and save it to a `program.asm` file.

```

addi    t0, zero, 0x55AA
stw     t0, 0x2000(zero)
break

```

- Select Nios II > Assemble to assemble the code. This will verify that the syntax is correct.
- Select File > Export to Hex File to generate the initialization file of your **ROM**. Save it in your `ROM.hex` that is in the quartus folder.
- Compile your Quartus project to update the **ROM** content. *If you want to update the ROM content without recompiling everything, select Processing > Update Memory Initialization File.*
- Program the FPGA and verify that the behavior is correct. If necessary, use ModelSim to look at the behavior in details. For that you will find a `tb_system.vhd` file that only generates a clock signal in the **testbench** folder. The simulation should take into account the memory initialization file, if it does not you probably specified incorrectly the path to the file.



To test the current (incomplete) **Controller** you should use the `test_Controller0.bat`. You can also use the other testbenches that are provided to verify other components once the controller is fully implemented. For that, open the modelsim folder and execute the corresponding batch files (for example, to test the Extend unit, execute the `test_Extend.bat` file).

- Modify the assembly program to test all of the instructions that you have implemented. For example, you can write a program that displays the result of an addition onto the LEDs.

## 4 Extending the multicycle CPU with flow control

In this section you will add flow control to the CPU. This will enable the CPU to do conditional jumps in the code with the *branches* instructions and to call procedures with the **call** and **ret** instructions. To implement these instructions, you will create three new *Execute* states (i.e., the states coming from **DECODE** and going to **FETCH1**) to the state machine. These three states are described in the following subsections.

### 4.1 BRANCH


The **BRANCH** state executes *branch* instructions, which are **I-Type** instructions.

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
A					B					IMM16																OP					

The following table describes the different *branch* instructions.

Instruction	Type	OP	Jumps to label if:
<b>br</b> label	I-type	0x06	<i>no condition</i>
<b>bge</b> rA, rB, label	I-type	0x0E	$rA \geq rB$
<b>blt</b> rA, rB, label	I-type	0x16	$rA < rB$
<b>bne</b> rA, rB, label	I-type	0x1E	$rA \neq rB$
<b>beq</b> rA, rB, label	I-type	0x26	$rA = rB$
<b>bgeu</b> rA, rB, label	I-type	0x2E	$(\text{unsigned})rA \geq (\text{unsigned})rB$
<b>bltu</b> rA, rB, label	I-type	0x36	$(\text{unsigned})rA < (\text{unsigned})rB$

During the **BRANCH** state, the **ALU** compares the values of the registers **a** and **b**. If the comparison is verified, the **PC** must take the value  $PC \leftarrow PC + 4 + IMM16$  ( $PC$  being the address of the current instruction). But remember that the **PC** has already been incremented by 4 during the state **FETCH2**. Therefore, we only need to add the signed *immediate* value to the current address stored in the **PC**.

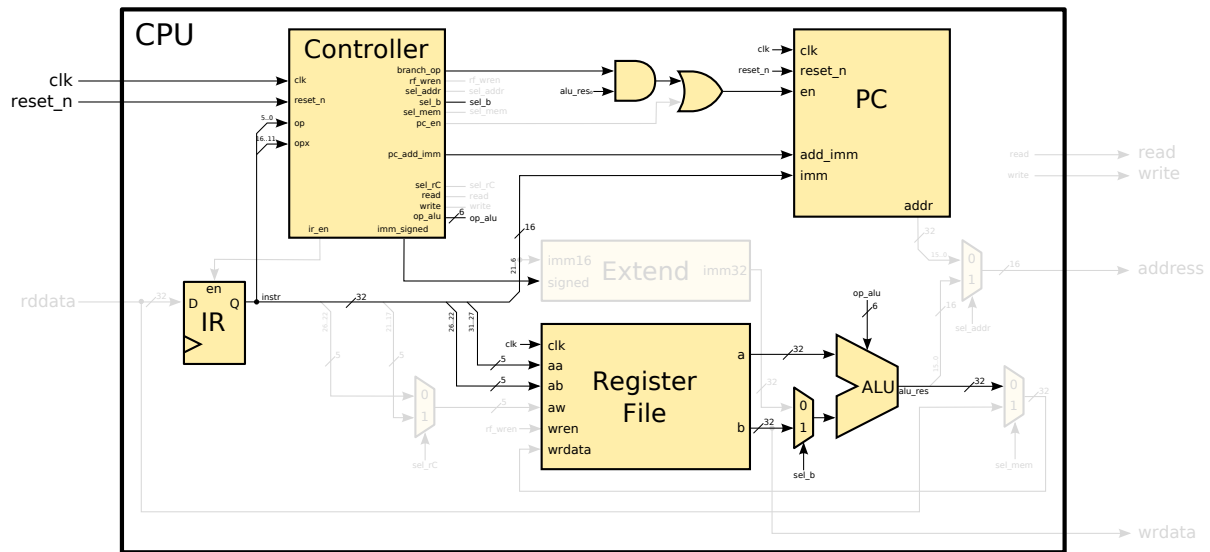

Here, some logical gates have been added so that when the **branch\_op** signal and the least significant bit of the result of the ALU are active, the **PC** is enabled. By default, the value that is added to the **PC** is 4. The **pc.add\_imm** signal tells to the **PC** to select the *immediate* value instead of 4 for the addition.

This is a small example of a loop made with a *branch* instruction:

```

    addi r2, r2, 32
loop:
    addi r2, r2, -1
    ...
    bge r2, r0, loop

```

## 4.2 CALL


The **CALL** state executes the **call** instruction, which is a **I-type** instruction with **OP**=0x00.

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0x00					0x00					IMM16												0x00									

The following table describes the **call** instruction.

Instruction	Type	OP	Description
<b>call</b> label	I-type	0x00	Call procedure label

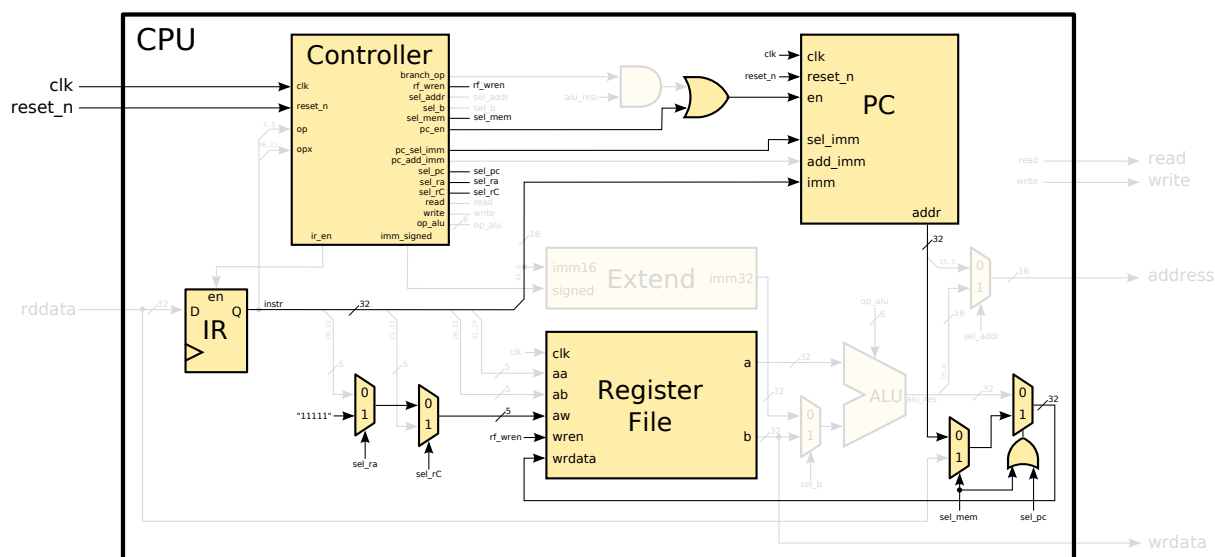During the **CALL** state, the current **PC** value is saved in the *return address* register (**ra**). The next address of **PC** is the value of the IMM16 field shifted to the left by 2.



The **pc\_sel\_imm** signal selects the immediate field as the next value of the **PC**. In the **call** instruction, the embedded address is word aligned. Since the **PC** is byte aligned, the immediate value must be shifted to the left by 2.

The multiplexer controlled by the **sel\_ra** signal selects the write address register from either the **B** instruction field or the address of the **ra** register (address 31 in the **Register File**).

### 4.3 JMP

The **JMP** state executes the **jmp** and **ret** instructions, which are **R-type** instructions with **OPX**=0x0D and **OPX**=0x05, respectively.

**jmp** instruction format:

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
A					0x00					0x00					0x0D					0x00					0x3A						

**ret** instruction format:


31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0x1F					0x00					0x00					0x05					0x00					0x3A						

Note that for the instruction **ret**, the field **A** is implicitly set to the register **ra** (address 31 in the **Register File**), and **ret** is equivalent to **jmp ra**.

The following table describes the **ret** and **jmp** instructions.

Instruction	Type	OPX	Description
<b>ret</b>	R-type	0x05	$PC \leftarrow ra$
<b>jmp</b> <i>ra</i>	R-type	0x0D	$PC \leftarrow rA$

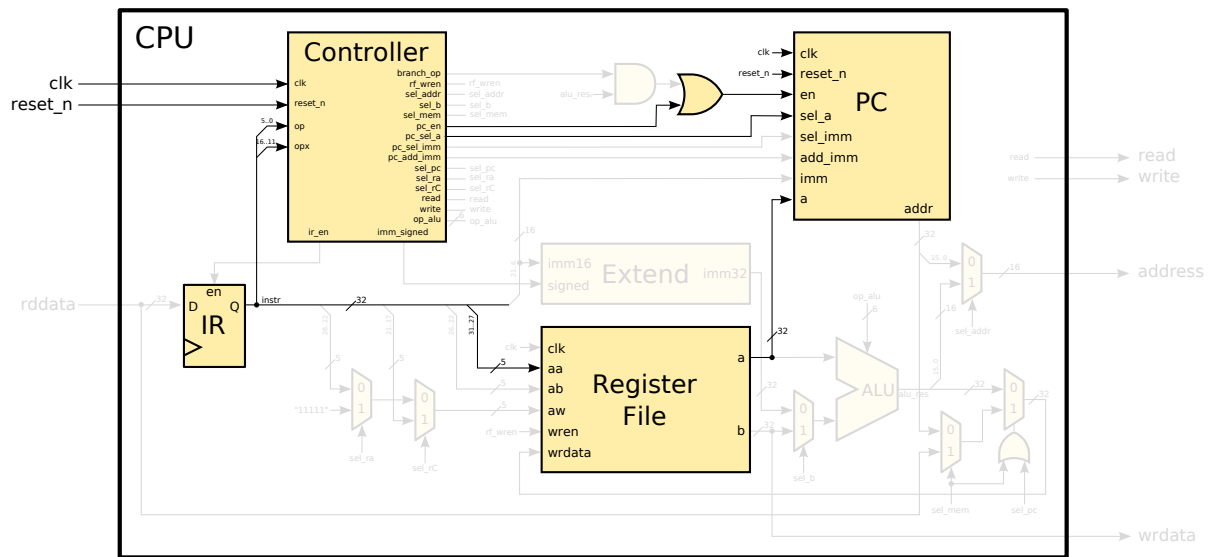During the **JMP** state, the **PC** address takes the value from the register **a**.



The **pc\_sel\_a** signal selects the value coming from the register **a** as the next value of the PC.

## 4.4 JMPI and CALLR Instructions

Read the descriptions of the `jmp_i` and `call_r` instructions and implement them.

### 4.4.1 JMPI

During a **jmp\_i** instruction, the PC takes the value of the immediate field shifted to the left by 2, as for the **call** instruction.

Instruction	Type	OP	Description
<b>jmp_i</b> label	I-type	0x01	Jumps to label

### 4.4.2 CALLR

During a **call\_r** instruction, the current PC address is saved in the **ra** register, and the next value of the PC takes its new value from the register **a**.

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
A					0x00					0x1F					0x1D					0x00									0x3A		

The field **C** of the **call\_r** instruction is implicitly set to **ra** (address 31 in the Register File).

Instruction	Type	OPX	Description
<b>call_r</b> rA	R-type	0x1D	$ra \leftarrow PC$ ; $PC \leftarrow rA$

## 4.5 Exercise

- In Quartus, modify the **Controller** and the **PC** to add flow control to your CPU.
- Compile and correct any errors that you find.
- Modify your assembly program `program.asm` to test the new instructions of the CPU.
- Generate the new `ROM.hex` file.
- Compile your Quartus project and program the FPGA. Use ModelSim for debugging.

## 5 Completing the Multicycle CPU with the Remaining Instructions

In this final section, you will complete your CPU with the remaining operations. Most of the work will be to generate, from the instruction, the correct value of the **op\_alu** signal. We will give you some hints to generate it efficiently.

### 5.1 Immediate Operations

The following table lists all the instructions that can be handled by the **I.OP** state:

Instruction	Type	OP	Description
<b>addi</b> <i>rB, rA, imm</i>	I-type	0x04	$rB \leftarrow rA + (\text{signed})imm$
<b>cmpgei</b> <i>rB, rA, imm</i>	I-type	0x08	$rB \leftarrow (rA \geq (\text{signed})imm)? 1 : 0$
<b>cmplti</b> <i>rB, rA, imm</i>	I-type	0x10	$rB \leftarrow (rA < (\text{signed})imm)? 1 : 0$
<b>cmpnei</b> <i>rB, rA, imm</i>	I-type	0x18	$rB \leftarrow (rA \neq (\text{signed})imm)? 1 : 0$
<b>cmpeqi</b> <i>rB, rA, imm</i>	I-type	0x20	$rB \leftarrow (rA = (\text{signed})imm)? 1 : 0$

The following *immediate* operations can not be handled by the **I.OP** state. The immediate value must be considered as an *unsigned* number. You will have to create a new *Execute* state for these instructions.

Instruction	Type	OP	Description
<b>andi</b> <i>rB, rA, imm</i>	I-type	0x0C	$rB \leftarrow rA \text{ and } (\text{unsigned})imm$
<b>ori</b> <i>rB, rA, imm</i>	I-type	0x14	$rB \leftarrow rA \text{ or } (\text{unsigned})imm$
<b>xori</b> <i>rB, rA, imm</i>	I-type	0x1C	$rB \leftarrow rA \text{ xor } (\text{unsigned})imm$
<b>cmpgeui</b> <i>rB, rA, imm</i>	I-type	0x28	$rB \leftarrow (\text{unsigned})rA \geq (\text{unsigned})imm$
<b>cmpltui</b> <i>rB, rA, imm</i>	I-type	0x30	$rB \leftarrow (\text{unsigned})rA < (\text{unsigned})imm$

### 5.2 Register Operations

The following tables lists all the instructions that can be handled by the **R.OP** state:

Instruction	Type	OPX	Description
<b>add</b> <i>rC, rA, rB</i>	R-type	0x31	$rC \leftarrow rA + rB$
<b>sub</b> <i>rC, rA, rB</i>	R-type	0x39	$rC \leftarrow rA - rB$
<b>cmpge</b> <i>rC, rA, rB</i>	R-type	0x08	$rC \leftarrow (rA \geq rB)? 1 : 0$
<b>cmplt</b> <i>rC, rA, rB</i>	R-type	0x10	$rC \leftarrow (rA < rB)? 1 : 0$
<b>cmpne</b> <i>rC, rA, rB</i>	R-type	0x18	$rC \leftarrow (rA \neq rB)? 1 : 0$
<b>cmpeq</b> <i>rC, rA, rB</i>	R-type	0x20	$rC \leftarrow (rA = rB)? 1 : 0$
<b>cmpgeu</b> <i>rC, rA, rB</i>	R-type	0x28	$rC \leftarrow ((\text{unsigned})rA \geq (\text{unsigned})rB)? 1 : 0$
<b>cmpltu</b> <i>rC, rA, rB</i>	R-type	0x30	$rC \leftarrow ((\text{unsigned})rA < (\text{unsigned})rB)? 1 : 0$
<b>nor</b> <i>rC, rA, rB</i>	R-type	0x06	$rC \leftarrow rA \text{ nor } rB$
<b>and</b> <i>rC, rA, rB</i>	R-type	0x0E	$rC \leftarrow rA \text{ and } rB$
<b>or</b> <i>rC, rA, rB</i>	R-type	0x16	$rC \leftarrow rA \text{ or } rB$
<b>xor</b> <i>rC, rA, rB</i>	R-type	0x1E	$rC \leftarrow rA \text{ xor } rB$
<b>rol</b> <i>rC, rA, rB</i>	R-type	0x03	$rC \leftarrow rA \text{ rol } rB_{4..0}$
<b>ror</b> <i>rC, rA, rB</i>	R-type	0x0B	$rC \leftarrow rA \text{ ror } rB_{4..0}$
<b>sll</b> <i>rC, rA, rB</i>	R-type	0x13	$rC \leftarrow rA \ll rB_{4..0}$
<b>srl</b> <i>rC, rA, rB</i>	R-type	0x1B	$rC \leftarrow (\text{unsigned})rA \gg rB_{4..0}$
<b>sra</b> <i>rC, rA, rB</i>	R-type	0x3B	$rC \leftarrow (\text{signed})rA \gg rB_{4..0}$

The following *shift* and *rotate* operations are R-type instructions, but use a small 5-bit immediate value for the second operand. These instructions can not be handled by the **R.OP** state. You will have to create a new *Execute* state for these instructions.

Instruction	Type	OPX	Description
<b>roli</b> <i>rC, rA, imm</i>	R-type	0x02	$rC \leftarrow rA \text{ rol } \text{imm}_{4..0}$
<b>slli</b> <i>rC, rA, imm</i>	R-type	0x12	$rC \leftarrow rA \ll \text{imm}_{4..0}$
<b>srli</b> <i>rC, rA, imm</i>	R-type	0x1A	$rC \leftarrow (\text{unsigned})rA \gg \text{imm}_{4..0}$
<b>srai</b> <i>rC, rA, imm</i>	R-type	0x3A	$rC \leftarrow (\text{signed})rA \gg \text{imm}_{4..0}$

### 5.3 Hint for the generation of the op\_alu signal

Look carefully at the **OP** or **OPX** fields of the instructions and compare it to the corresponding **ALU** opcode:

- For **I-type** instructions, the 3 most significant bits of the **OP** field can directly be mapped on the 3 least significant bits of the **op\_alu** signal.
- For **R-type** instructions, the 3 most significant bits of the **OPX** field can directly be mapped on the 3 least significant bits of the **op\_alu** signal.
- Don't take into account the instructions that do not use the **ALU**, this will simplify the generation of **op\_alu**.

### 5.4 Exercise

- Complete the **Controller** to implement these remaining instructions.
- Compile and correct any error.
- Modify your assembly program `program.asm` to test some of the new instructions.
- Generate the new `ROM.hex` file.
- Compile your Quartus project and program the FPGA. Use ModelSim and the testbenches that are provided for debugging.

## 6 Optimizing the state machine

Look at the state machine of the **Controller**. Is it always necessary to go back to **FETCH1** after the execution of an instruction? For example, from **I.OP**, could we directly go to **FETCH2**?

### 6.1 Exercise

- Explain why and how.
- Modify the **Controller** to bypass **FETCH1** when it is possible.

## 7 Submission

Submit all vhdl files related to the exercises in sections 3, 4.5, 5.4 and 6.1 (`CPU.vhd`, `IR.vhd`, `PC.vhd`, `System.vhd`, `buttons.vhd`, `controller.vhd`, `extend.vhd`, `mux2x16.vhd`, `mux2x32.vhd` and `mux2x5.vhd`) and the required files from the previous labs (`ALU.vhd`, `add_sub.vhd`, `comparator.vhd`, `logic_unit.vhd`, `multiplexer.vhd`, `register_file.vhd` and `shift_unit.vhd`).